

KATHMANDU UNIVERSITY
End Semester Examination [C]
November, 2018

Marks scored:

Level : B.E./ B.Sc.

Year : II

Course : EEG 202

Semester: I

Exam Roll No. :

Time: 30 mins

F.M. : 20

Registration No.:

Date :


NOV 15 2018

SECTION "A"
[20×1=20 marks]

Choose the most appropriate option. Symbols have their usual meaning.

- If three input NOR gate has eight input possibilities, how many of those possibilities will result high output?
a. 1 b. 2 c. 3 d. 7
- The binary equivalent of decimal number 41.6875 is _____
a. 101000.1011 b. 101001.1010 c. 101011.101 d. 101001.1011
- If A and B are not inputs to the two input X-NOR gate, which of the following expression for output is correct?
a. $\bar{A}B + A\bar{B}$ b. $\bar{A}\bar{B} + A\bar{B}$ c. $\bar{A}B - A\bar{B}$ d. $\bar{A}\bar{B} + AB$
- Which of the following Boolean postulate is true?
a. $X + 1 = X$ b. $X + 1 = 1$ c. $X + 1 = 1$ d. $X + 1 = 0$
- TTL operates from a _____
a. 12 - Volt supply b. 9 - Volt supply c. 5 - Volt supply d. 3 - Volt supply
- 2's complement of decimal number 1101100 is given by
a. 1010100 b. 0010100 c. 0010101 d. 0010000
- Which of the following expression represents the Simplified Boolean function for the function $F(A,B,C) = \sum(1,2,3,5,7)$
a. $F = A + \bar{A}B$ b. $F = A + AB$ c. $F = A + \bar{C}B$ d. $F = B + \bar{A}B$
- Which of the following is universal logic gate?
a. AND b. OR c. AND d. NAND
- Which of the following binary combination represents the result of BCD addition of two BCD numbers 0100 and 1000?
a. 10010 b. 0 1100 c. 10001 d. 10111
- A ROM internally includes programmable OR gates and _____
a. AND gates b. X-OR gates c. An encoder d. A Decoder
- Flip flop conversion expressions for D flip flop to T flip flop is given by
a. $D = T\bar{Q} + \bar{T}Q$ b. $D = T\bar{Q} + Q$ c. $D = T\bar{Q} + \bar{T}$ d. $D = T\bar{Q} + \bar{T}\bar{Q}$
- The characteristic equation for the T flip flop is given by
a. $Q(t+1) = J\bar{Q} + KQ$ b. $Q(t+1) = J\bar{Q} + \bar{K}Q$
c. $Q(t+1) = \bar{J}\bar{Q} + \bar{K}\bar{Q}$ d. $Q(t+1) = \bar{J}\bar{Q} + \bar{K}Q$

 13. The following figure represents the state transition diagram of _____



- a. SR flip-flop b. D flip-flop c. T flip-flop d. JK flip-flop
14. For JK flip flop with $J=1$, $K=1$, the output after clock pulse will be _____
 a. Low b. High c. No change d. Complimented
15. An encoder has maximum _____ input lines for N output lines.
 a. N b. N^2 c. 2^N d. $N-1$
16. A 3 bit synchronous up counter counts up to _____
 a. 3 b. 6 c. 7 d. 8
17. Mod-6 asynchronous up counter requires _____ flip flops.
 a. 6 b. 5 c. 4 d. 3
18. Which of the following expression is correct for the given K-Map?

| AB\CD | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 00 | 1 | 1 | 0 | 0 |
| 01 | 1 | 1 | 0 | 0 |
| 11 | 1 | 1 | 0 | 0 |
| 10 | 1 | 1 | 0 | 0 |

- a. $F = \bar{A}$ b. $F = \bar{B}$ c. $F = \bar{C}$ d. $F = \bar{D}$
19. BCD input 0110 is fed to a seven segment display through BCD to seven segment decoder/driver. The segments which will lit up are:
 a. a,b,d,e,f b. a,b,c,d,e,f c. all d. a,c,d,e,f,g
20. A 5 bit serial input serial output shift register requires
 a. 4 SR flip flops b. 5 JK flip c. 5 D flip flops d. 4 D flip flops

KATHMANDU UNIVERSITY
End Semester Examination [C]
November, 2018

NOV 15 2018
Course : EEG 202
Semester: II
F.M. : 55

Level : B.E./ B.Sc.
Year : II
Time : 2 hrs. 30 mins.

SECTION "B"

[5 Q.×11=55 marks]

Attempt any FIVE questions.

Figure in the margin indicates the full mark. Students are required to answer in their own words as far as practicable.

1.
 - a. Differentiate between half adder and full adder and design logic circuit for full adder. [6]
 - b. Using 10's complement, subtract (a) 3250 – 72532 (b) 72532-3250 [3]
 - c. Verify the Boolean expression, $x + yz = (x+y)(x+z)$ [2]
2.
 - a. Simplify the following Boolean function using K-map
 $F(w,x,y,z) = \sum(0,1,2,4,5,6,8,9,12,13,14)$ and implement the resulting expression with NOR gates. [6]
 - b. Draw truth table and design 4 to 1 line multiplexer circuit. [5]
3.
 - a. Construct 4X16 decoder with two 3X8 decoder. [3]
 - b. Design logic circuit for 3 bit gray code to binary converter. [3]
 - c. Describe the working of serial in serial out shift register with circuit diagram and timing diagram. [5]
4.
 - a. Design a logic circuit that has four inputs W, X, Y, Z and an output that is to be high only when input Z is low and at the same time other any two inputs are high. [6]
 - b. Draw the state transition diagram of SR flip-flop and D flip-flop. [2]
 - c. Implement the following Boolean functions using ROM
 $F_1(A,B,C) = \sum(0,1,2,4)$ and $F_2(A,B,C) = \sum(0,5,6,7)$ [3]
5.
 - a. Design a logic circuit for mod-8 synchronous up counter and explain the operation using timing diagram. [5]
 - b. Draw the characteristic table and excitation table for JK flip-flop. With the help of conversion expression, construct T flip-flop from the D flip-flop. [6]
6.
 - a. Design a logic circuit for mod-6 asynchronous up/down counter and explain the operation. [5]
 - b. A sequential circuit has two D flip-flops A and B, one input X and output Y. The circuit is described by the following flip-flop input output equations:
 $D_A = AX+BX$, $D_B = AX + B'X$ and $Y = AB$. Draw the state table and state diagram of the circuit. [6]

